$$\frac{dV}{dx} = -(R+j\omega L) I \rightarrow \frac{d^{2}v}{dx^{2}} = \int^{2}v$$

$$\frac{dI}{dx} = -(G+j\omega C) V \rightarrow \frac{d^{2}I}{dI^{2}} = \int^{2}I$$

$$\sqrt{=x+j\beta} = \sqrt{(x+j\omega)} (G+j\omega)$$

a- Nepers /m , Inep/m - 8.68 68/m

$$Z_{o} = \sqrt{\frac{(R+j\omega L)}{(G+j\omega c)}}$$

Loss less: 
$$\alpha = 0 \Rightarrow R = 0$$
,  $G = 0$ 

$$V = \hat{J}\omega\sqrt{LC} , Z_{o}(real) = \sqrt{\frac{L}{C}} , \vartheta p^{-3\times10^{8}} m/s$$

Distortion (ens:

- Erual raise and fall time

- series time constant = shunt time constant

$$\begin{array}{cccc} & & & & & & \\ & & & & & \\ & & & & \\ & & & & \\ & & & & \\ & & & \\ & & & \\ & & & \\ & & & \\ & & & \\ & & & \\ & & & \\ & &$$

-  $\alpha$  depends on  $\omega$   $\rightarrow$  delay distortion  $\beta$  depends on  $\omega$   $\rightarrow$  free. distortion

Reflection coefficient  $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$ 

VSWR: 
$$P = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$
 Sic inductance  $0.0$  C  $0.0$ 

$$Z_{l} = \begin{cases} jZ_{0} \tanh \beta l & \rightarrow s \cdot c \\ -jZ_{0} \coth \beta l & \rightarrow o \cdot c \end{cases} \qquad Z_{l} \Rightarrow \frac{\sqrt{4}, \sqrt{4}}{2} Z_{l}$$

$$Z_{l} = \frac{Z_{0}}{Z_{l}}$$